Name:	Date:	Per:

Electricity and Magnetism Worksheet

- 1. When a plastic rod is rubbed with fur, the plastic rod becomes negatively charged. Which statement explains the charge transfer between the plastic rod and the fur?
 - a) Protons are transferred from the plastic rod to the fur.
 - b) Protons are transferred from the fur to the plastic rod.
 - c) Electrons are transferred from the plastic rod to the fur.
 - d) Electrons are transferred from the fur to the plastic rod.
- 2. A series circuit has a 6-V battery and 3 ohms of resistance. How much current will flow through the circuit?
- 3. What voltage is required to run a 45-watt light bulb if the current is 0.5 amphere?
- 4. How much current is used by a 120-V refrigerator that uses 650 W of power?
- 5. Which *best* describes a circuit in series?
 - a) Different parts are on separate branches.
 - b) Current values are different at various points in the circuit.
 - c) Electrons may take several paths.
 - d) Electrons have only one path at all times.

- 6. Which statement is true about parallel circuits?
 - a) A They contain separate branches through which current can flow.
 - b) They are usually called open circuits.
 - c) They provide one path through which current can flow.
 - d) They cease to function when one part of the circuit is disconnected.
- 7. A motor has a current of 2 A flowing through it when it is powered with a 12-V battery. What is the power (wattage) used by the motor?
- 8. A sheet of paper is positioned to completely cover a bar magnet. Iron filings are then gently sprinkled on the paper. What does the pattern created by the iron filings indicate?
 - a) the stronger of the two poles
 - b) the distance between the two poles
 - c) the midpoint of the area between the two poles
 - d) the magnetic field created by the two poles
- 9. Which statement is true about parallel circuits?
 - a) A They contain separate branches through which current can flow.
 - b) They are usually called open circuits.
 - c) They provide one path through which current can flow.
 - d) They cease to function when one part of the circuit is disconnected.